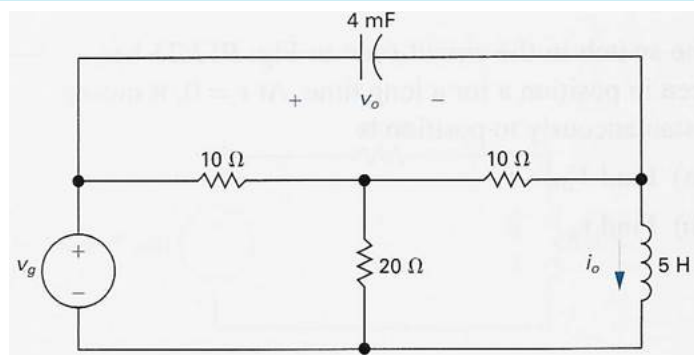


Started on Sunday, 31 March 2019, 12:08 PM**State** Finished**Completed on** Sunday, 31 March 2019, 12:09 PM**Time taken** 1 min 39 secs**Grade** 100.00 out of 100.00**Question 1**

Correct

Mark 10.00 out of 10.00



P13.27a_6ed

There is no energy stored in this circuit for $t < 0$.Given that $v_g(t) = 75 u(t)$ for $t \geq 0$.a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V_o(s) = \boxed{375} / [s(s + \boxed{5})]$$

b) Find the time domain $v_o(t)$.

$$v_o(t) = \boxed{75} [1 - \exp(-\boxed{5} t)] u(t) \text{ V}$$


Correct

Marks for this submission: 10.00/10.00.

Question 2

Correct

Mark 10.00 out of 10.00

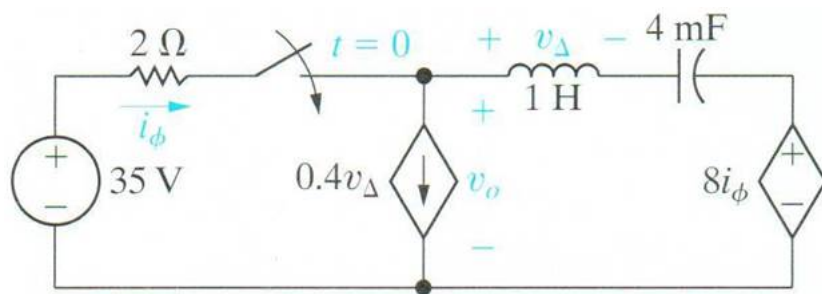

P13.13_6ed and P13.15_7ed

Given: No energy is stored in this circuit for $t < 0$.At time $t = 0$, the switch closes (i.e. makes contact).a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the voltage $v_o(t)$.

$$V(s) = \boxed{35} / s + (\text{mag } \boxed{2.863} \text{ Angle } \boxed{167}^\circ) / (s + 1 - j 7) + (\text{mag } \boxed{2.86} \text{ Angle } \boxed{-167}^\circ) / (s + 1 + j 7)$$

b) Find the inverse transform to find the time domain $v_o(t)$.

$$v_o(t) = [\boxed{35} + \boxed{5.78} \exp(-\boxed{1} t) \cos(\boxed{7} t + \boxed{167}^\circ)] u(t) \text{ V}$$


Correct

Marks for this submission: 10.00/10.00.

Question 3

Correct

Mark 10.00 out of 10.00

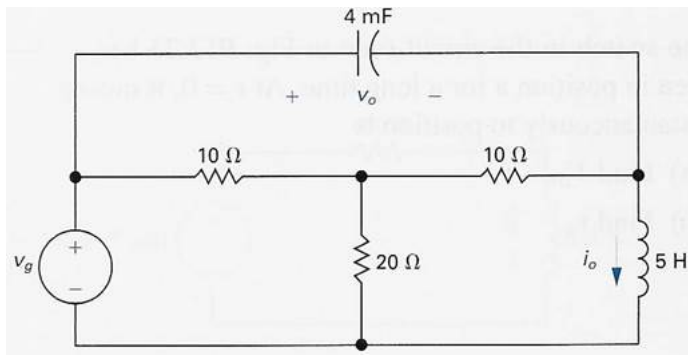

P13.27b_6ed

There is no energy stored in this circuit for $t < 0$.

Given that $v_g(t) = 75 u(t)$ for $t \geq 0$.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the current $i_o(t)$.

$$I_o(s) = 15 / [s(s + 5)]$$

b) Find the time domain $i_o(t)$.

$$i_o(t) = 3 [1 - \exp(-5t)] u(t) \text{ A}$$


Correct

Marks for this submission: 10.00/10.00.

Question 4

Correct

Mark 10.00 out of 10.00

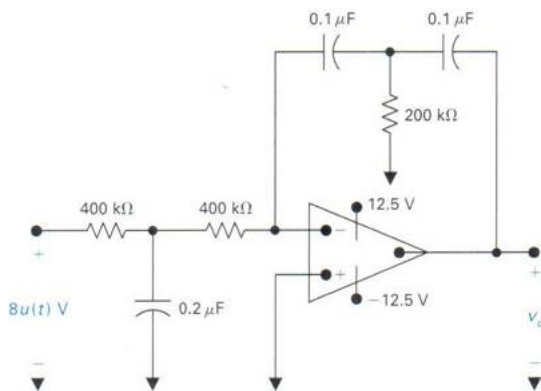

P13.46_6ed

Given: No energy is stored in this circuit for $t < 0$ and you can assume the OpAmp is ideal.

a) For $t > 0$, Redraw this circuit in the frequency domain and find the Laplace form of the output voltage $v_o(t)$.

$$V_o(s) = -5000 / s^3$$

b) Find the inverse transform and then determine the time domain output voltage $v_o(t)$.

$$v_o(t) = -2500 t^2 u(t) \text{ V}$$

c) Calculate how long in ms (milli sec) until the opamp saturates.

$$t_{\text{saturation}} = 70.7 \text{ ms (milli sec)}$$


Correct

Marks for this submission: 10.00/10.00.

Question 5

Correct

Mark 10.00 out of 10.00

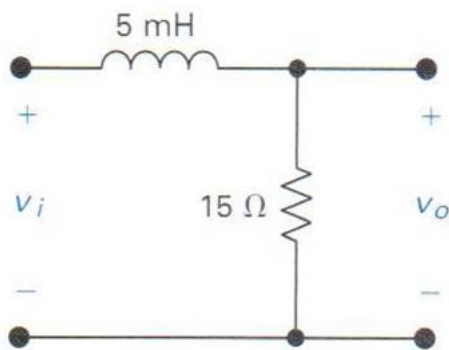

P13.49d_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \boxed{3000} \checkmark / (s + \boxed{3000} \checkmark)$$


Correct

Marks for this submission: 10.00/10.00.

Question 6

Correct

Mark 10.00 out of 10.00

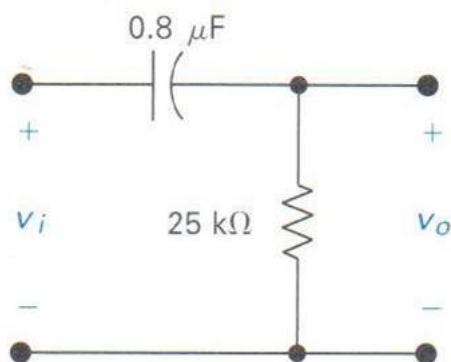

P13.49b_6ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = s / (s + \boxed{50} \checkmark)$$


Correct

Marks for this submission: 10.00/10.00.

Question 7

Correct

Mark 10.00 out of 10.00

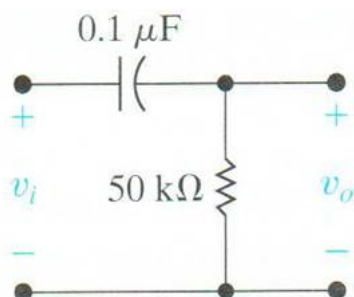

P13.49b_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = s / (s + \boxed{200} \checkmark)$$


Correct

Marks for this submission: 10.00/10.00.

Question 8

Correct

Mark 10.00 out of 10.00

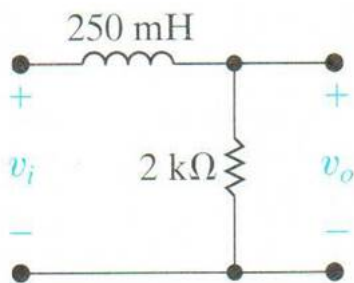

P13.49d_7ed

Find the s domain transfer function $H(s) = V_o/V_i$ for this circuit.

$$H(s) = \boxed{8000} / (s + \boxed{8000})$$


Correct

Marks for this submission: 10.00/10.00.

Question 9

Correct

Mark 10.00 out of 10.00

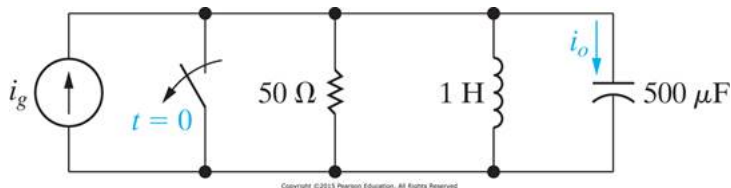

P13.56_10ed

There is no energy stored in this circuit at the time the switch is opened. The sinusoidal current source is generating the signal $25 \cos(200t)$ mA (milli Amp). The desired response signal is the current $i_o(t)$.

a) Find the s domain transfer function $H(s) = I_o/I_g$ for this circuit.

$$H(s) = s^2 / (s^2 + \boxed{40} s + \boxed{2000})$$

b) Find the s domain form for $I_o(s)$.

$$I_o(s) = \boxed{.025} s^3 / (\text{There are four factors in the denominator – list each one separately})$$

$$\text{Factor 1: } s + 20 - j \boxed{40}$$

$$\text{Factor 2: } s + 20 + j \boxed{40}$$

$$\text{Factor 3: } s + 0 - j \boxed{200}$$

$$\text{Factor 4: } s + 0 + j \boxed{200}$$

c) Find the time domain form $i_o(t)$.

$$i_o(t) = [\boxed{1.44} \exp(\boxed{-20} t) \cos(\boxed{40} t + \boxed{-97.9}^\circ) + \boxed{26} \cos(\boxed{200} t + \boxed{11.9}^\circ)] u(t) \text{ mA (milli A)}$$


Correct

Marks for this submission: 10.00/10.00.

Question 10

Correct

Mark 10.00 out of 10.00

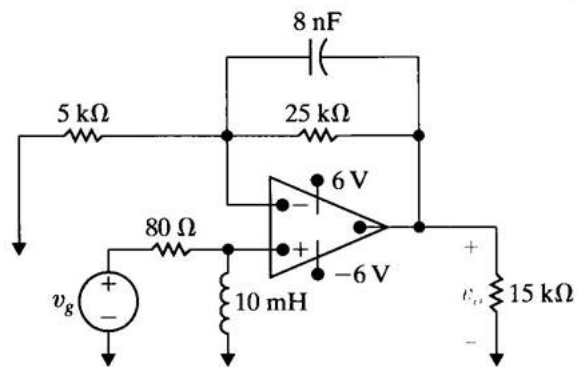

P13.78_7ed and P13.77_10ed

You may assume the opamp is ideal.

a) Find the s domain transfer function $H(s) = V_0/V_g$ for this circuit.

$$H(s) = s * (s + \boxed{30000}) / [(s + 5,000) * (s + \boxed{8000})]$$

b) Find the time domain $v_0(t)$ if $v_g(t) = 600 u(t)$ mV (milli V).

$$v_0(t) = [\boxed{5} e^{-5,000t} + \boxed{-4.4} \exp(\boxed{-8000} t)] u(t) \text{ V}$$

c) Find the steady-state express for $v_0(t)$ if $v_g(t) = 2 \cos(10,000 t)$ V.

$$v_0(t)_{\text{steady-state}} = [\boxed{4.42} \cos(\boxed{10000} t + \boxed{-6.3}^\circ)] u(t) \text{ V}$$

Correct

Marks for this submission: 10.00/10.00.

◀ Homework 8 - Chapter 12

Jump to...

Homework 10 - Bode Diagrams ▶