

[Home](#) ► [My courses](#) ► [EEE117-2019S-Sec1](#) ► [Exams and Quizzes](#) ►  
[Quiz 1 - Chapter 9](#)

---

<b>Started on</b>	Wednesday, 30 January 2019, 9:39 AM
-------------------	-------------------------------------

---

<b>State</b>	Finished
--------------	----------

---

<b>Completed on</b>	Wednesday, 30 January 2019, 9:59 AM
---------------------	-------------------------------------

---

<b>Time taken</b>	19 mins 58 secs
-------------------	-----------------

---


<b>Grade</b>	<b>100.00</b> out of 100.00
--------------	-----------------------------

---

## Question 1

Correct

Mark 100.00 out of 100.00

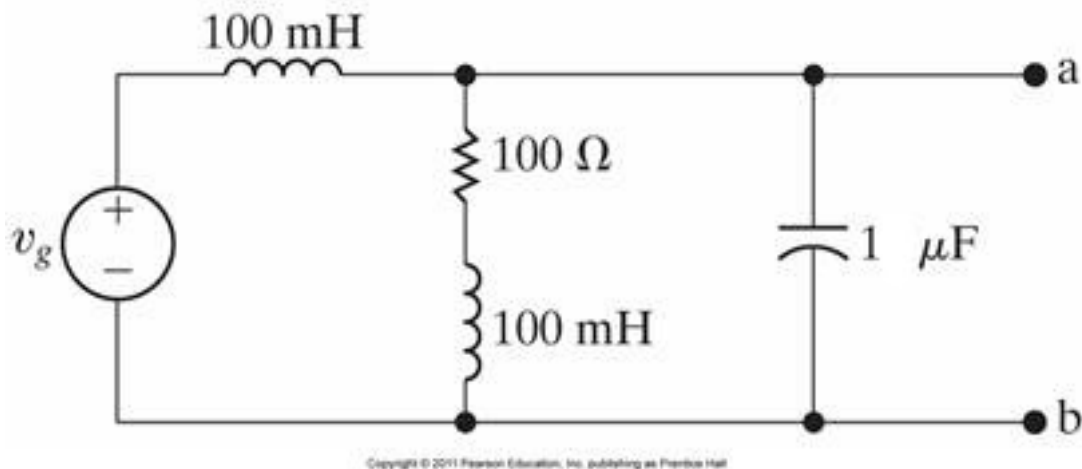

### Quiz 1d

The sinusoidal voltage source in the circuit  $v_g = 240 \cos(5,000t) \text{ V}_{\text{rms}}$ .

a) Find the Thévenin voltage with respect to the terminals a,b.

Express your answer in polar form (make the magnitude positive and the angle negative).

$$|V_{\text{Th}}| = \boxed{593.6} \checkmark \text{ V}$$

$$\text{Angle} = \boxed{-160.35} \checkmark ^\circ \text{ (Degrees)}$$

b) Find the Thévenin impedance with respect to the terminals a,b.

Express your answer in polar form (make the magnitude positive and the angle negative).

$$|Z_{\text{ab}}| = \boxed{874.5} \checkmark \Omega \text{ (Ohm)}$$

$$\text{Angle} = \boxed{-70.35} \checkmark ^\circ \text{ (Degrees)}$$

**Correct**

Marks for this submission: 100.00/100.00.

◀ Homework 14 - Chapter 16

Jump to...



Quiz 2 - Chapter 9 ▶